



CS2008 Numerical Computing

Assignment No: 04	CLO:
	Semester: Fall 2024
Due date: As of GCR date	Marks: 10 x5 = 50

Instructions

1. **Plagiarized work will result in zero marks.**
2. **No retake or late submission will be accepted.**
3. The submission should be a SINGLE UNZIPPED NOTEBOOK submitted on google classroom.
4. This notebook should properly document what you did? How you did it? And the source-code for each part as well as the generated outputs.
5. Your submission file should be according to the following **format: id_section_A2** e.g., i22123456_A_A2. (Note: A2 in the end denotes Assignment 2).

. Consider the electric circuit depicted in Figure

- (a) Analyze the particular circuit using Kirchhoff's laws, and form a linear system with 8 equations and 8 unknowns.
- (b) Solve the linear system using dense matrix techniques. Verify that your solution satisfies all the equations derived from Kirchhoff's laws.
- (c) Solve the linear system using sparse matrix techniques and absolute error tolerance 10^{-6} .
- (d) Compare the speed of the two numerical methods and say which one is faster.
- (e) Compute the difference of the two solutions and describe their accuracy.

